

ASSIGNMENT 5


QUESTION 1

Part A

Table has all the specifications

Parameters/ Components Used	Value
Closed Loop DC Gain (K)	13
Closed Loop BandWidth (fb)	13 MHz
Gm1	1.06 mS
Gm2	3.63 mS
Ci1	53 fF
Co1	53 fF
Ro1	94339.62 ohm
Ci2	0.1815 pF
Co2	0.1815 pF
Ro2	27548.209 ohm
CL	13 pF
Cc	1 PF
RL	1883.48 Ohms
Ri	17Kohms

Wu,loop	81681408.99 rad/sec
P2(non-dominant Pole)	326725636 rad/sec

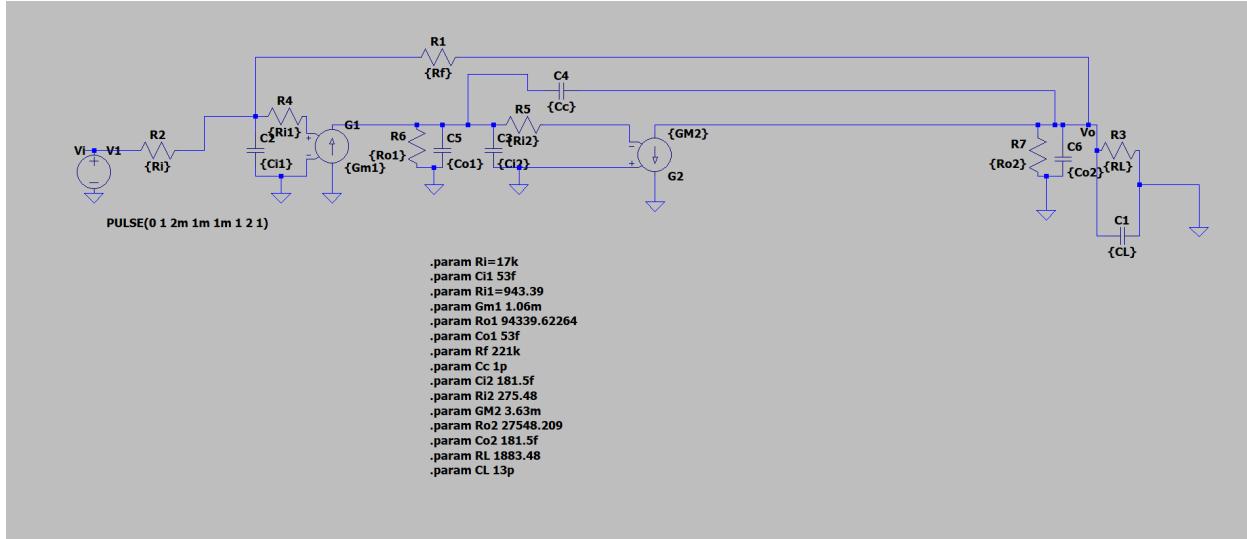

Schematic for Q1

```

.sparam Rin 17k
.sparam C1 53f

.sparam Gm1 1.06m
.sparam Ro1 94339.62264
.sparam Co1 53f
.sparam Rf 221k
.sparam Cc 1p
.sparam C12 181.5f

.pparam GM2 3.63m
.pparam Ro2 27548.209
.pparam Co2 181.5f
.pparam RL 1883.48
.pparam CL 13p

```

Parameters assigned
Hand Calculations

Tutorial-5

①

$$K = 13$$

$$\frac{\text{closed loop}}{\text{DC gain}} = -13$$

Closed loop band width

$$\omega_B = 13 \text{ MHz}$$

$$\text{Load Capacitor } C_L = 57 \text{ pF} = 13 \text{ pF}$$

$$\text{load resistance } R_L = \frac{10^6}{2\pi \times 13} = \cancel{1333 \text{ fF}}$$

Input resistance

$$R_i = 17 \text{ k}\Omega$$

$$C_C = 1 \text{ pF}$$

Closed loop bandwidth

$$P_2 = 4 \times (\omega_{\text{loop}})$$

$$G_i = G_o = \frac{G_m}{\omega_T} \quad \omega_T = 2 \times 10^{10}$$

$$G_{\text{loop}} = \frac{G_m}{100} \quad L_N = \frac{1}{G_m}$$

② closed loop bandwidth


loop gain \downarrow

unity

$$= 2\pi \times 13 \times 10^6$$

$$= 81681402.05 \text{ rad/sec}$$

$$4\omega_u = P_2$$

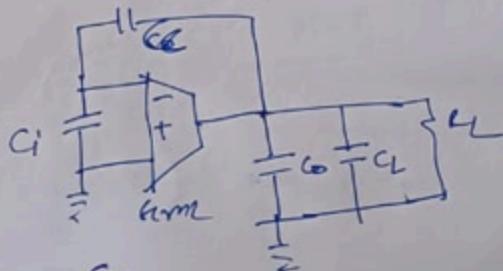

$$P_2 = \frac{\frac{1}{R_L} + \frac{C_C}{C_i + C_C}}{C_0 + Q + \frac{C_C C_i}{C_C + C_i}}$$

$$y_L = \frac{1}{R_L} + \frac{C_C G_m}{C_C + \frac{G_m}{\omega_T}}$$

$$\frac{\left(C_C + \frac{G_m}{\omega_T} \right) + C_C \left(\frac{G_m}{\omega_T} \right)}{C_C + \frac{G_m}{\omega_T}}$$

$$A_{VU} = \frac{C_C + \frac{G_m}{\omega_T}}{R_L} + C_C G_m$$

$$C_C \left(\frac{G_m}{\omega_T} \right) + \left(C_C + \frac{G_m}{\omega_T} \right) \left(C_C + \frac{G_m}{\omega_T} \right)$$

$$A_{VU} \left[C_C \frac{G_m}{\omega_T} + C_C G_m + (C_C + C_L) \frac{G_m}{\omega_T} + \frac{G_m^2}{\omega_T^2} \right] = G_m C_C + \frac{C_C}{R_L} + \frac{G_m}{R_L \omega_T}$$

$$\left(\frac{\omega_T}{\omega_T^2} \right) G_m^2 + 4 \left(2C_C + C_L \right) \frac{G_m}{\omega_T} + \left[- \frac{C_C}{\omega_T R_L} - \frac{C_C}{\omega_T^2} \right] + \left(A_{VU} C_C C_L - \frac{C_C}{R_L} \right) = 0$$

$$\cancel{A_{VU}} \frac{\omega_T}{\omega_T^2}$$

$$4 \times \frac{81681408.99}{4 \times 10^{20}} G_m^2 + G_m \left[4 \times \left[5 \times 10^{-12} \right] \times \frac{81681408.99}{2 \times 10^{20}} \right]$$

$$- 10^{-12} \times \frac{1}{241.74 \times 2 \times 10^{20}}$$

$$+ 4 \times \frac{81681408.99}{10^{-24} \times 13} - \frac{10^{-12}}{241.74 \times 2} = 0$$

$$\frac{Gm_1}{K_{CC}} = \omega_{loop}^2 r = 81681408 \cdot 0.99$$

$$Gm_1 = 81681408 \cdot 0.99 \times 1.5 \times 10^{-12}$$

$$= 1.06 \times 10^{-3}$$

$$Gm_2 = \sqrt{3.63 \times 10^{-3} / 1.2531}$$

$$R_p = K_{RL}$$

$$= 1.3 \times 17 K \cdot R$$

$$= 221 K \cdot R$$

①

$$\left[\begin{array}{l} C_1 = \frac{Gm_1}{\omega_T} \\ C_0 = \frac{Gm_1}{\omega_T} \end{array} \right] \quad \left[\begin{array}{l} 5.3 \times 10^{-14} \\ R_{01} \end{array} \right] \quad R_{N1} = 23.39$$

$$= 94339.62262$$

②

$$\left[\begin{array}{l} C_1 = \frac{Gm_2}{\omega_T} = 1.915 \\ C_0 = \frac{Gm_2}{\omega_T} = 1.915 \times 10^{-3} \end{array} \right] \quad R_{02} = \frac{27598.205}{R_{N2}} = 275.98$$

B) LOOP GAIN and Phase Margin

Schematic:

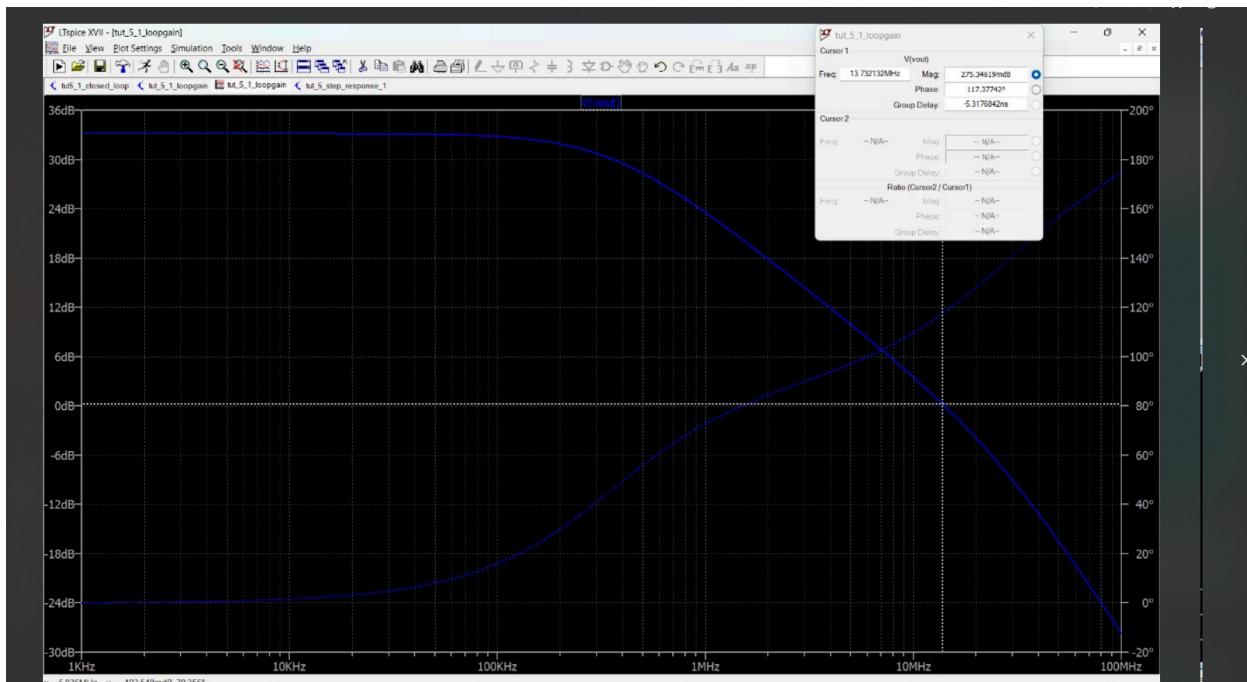
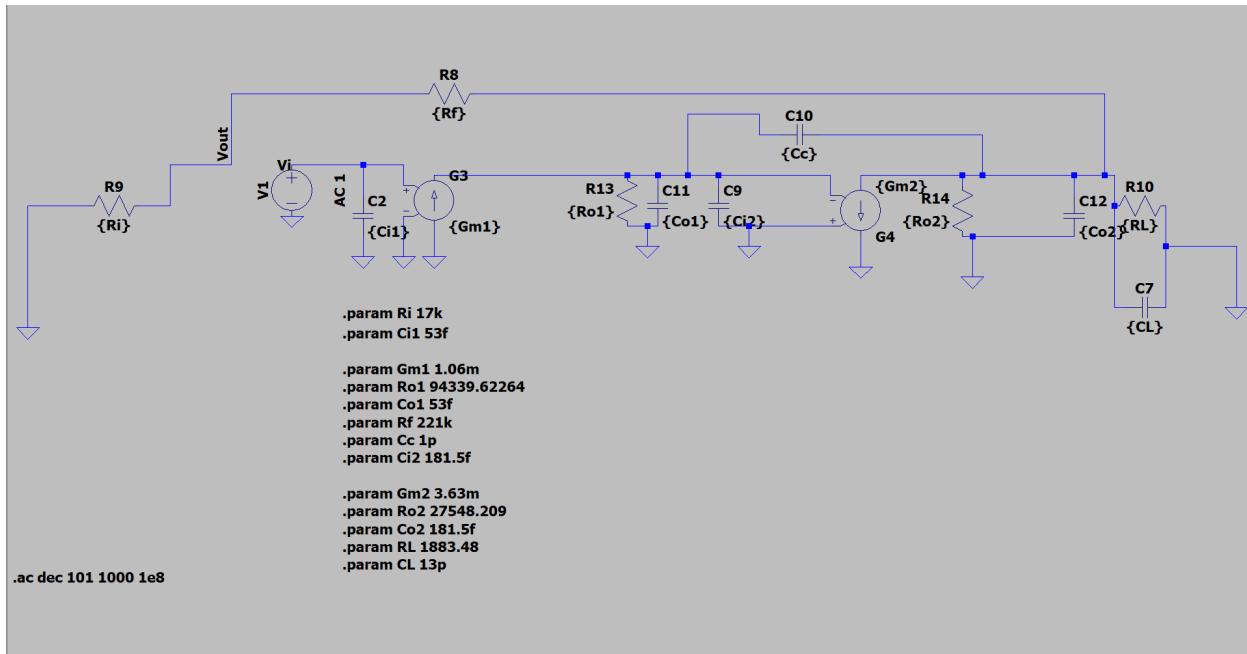


Fig 1: Magnitude and Phase of Loop Gain vs Frequency

It can be observed that the unity gain frequency is equal to approximately 13.7321 MHz (close to 13 MHz)

And the observed phase Margin at the loop gain frequency is equal to $180 - 117.3 = 62.7$ degrees

C) Closed Loop Transfer Function

Schematic:

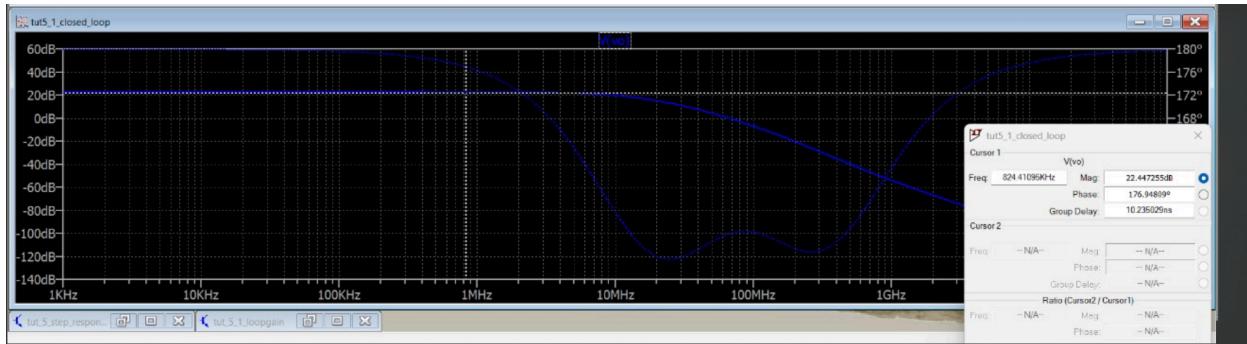
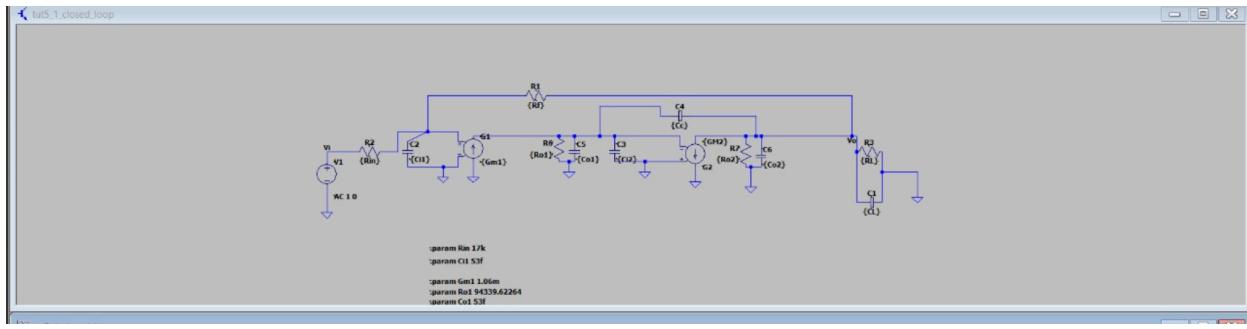


Fig 2

It can be observed from fig 2, that DC gain of the closed loop is equal to 22.447 which is corresponding to a magnitude of 13.25 (approximately 13, which is the desired one).

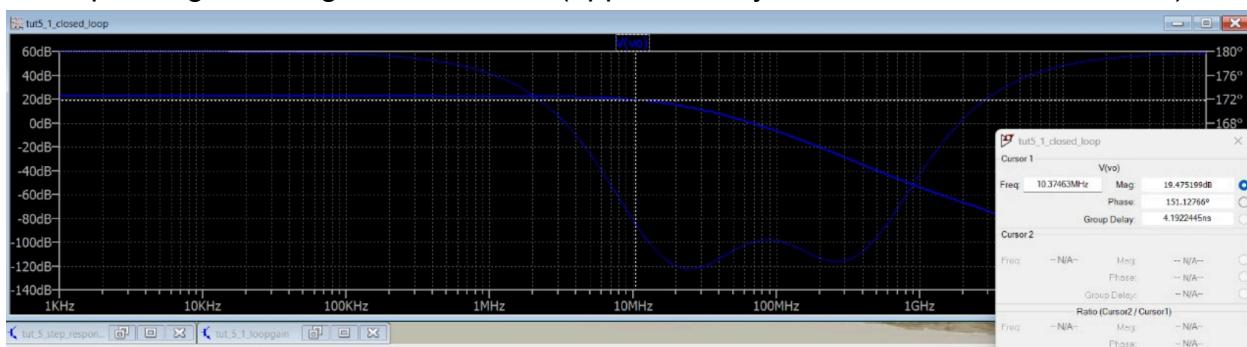


Fig 3

From fig 3, we can see that the 3-dB Bandwidth is equal to 10.37 MHz, which is close to the requirement of the question(3 dB bandwidth= 13MHz and DC gain=k=13)

D) Unit Step Response:

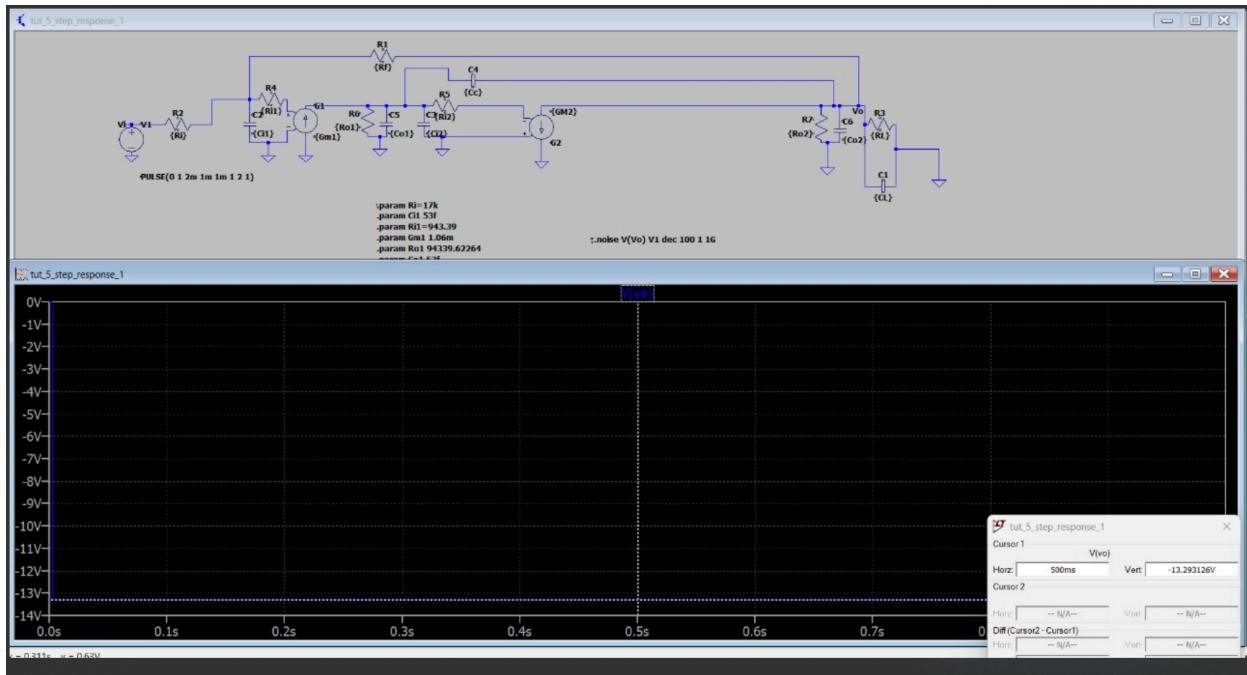


Fig 4: Unit step Response

A unit step is applied with the help of a pulse function in the input at the output with respect to time is a DC Voltage of -13.29 Volts, so there is a steady error of 0.29 volts (as the desired one is -13 volts)

E) Output and Input referred noise

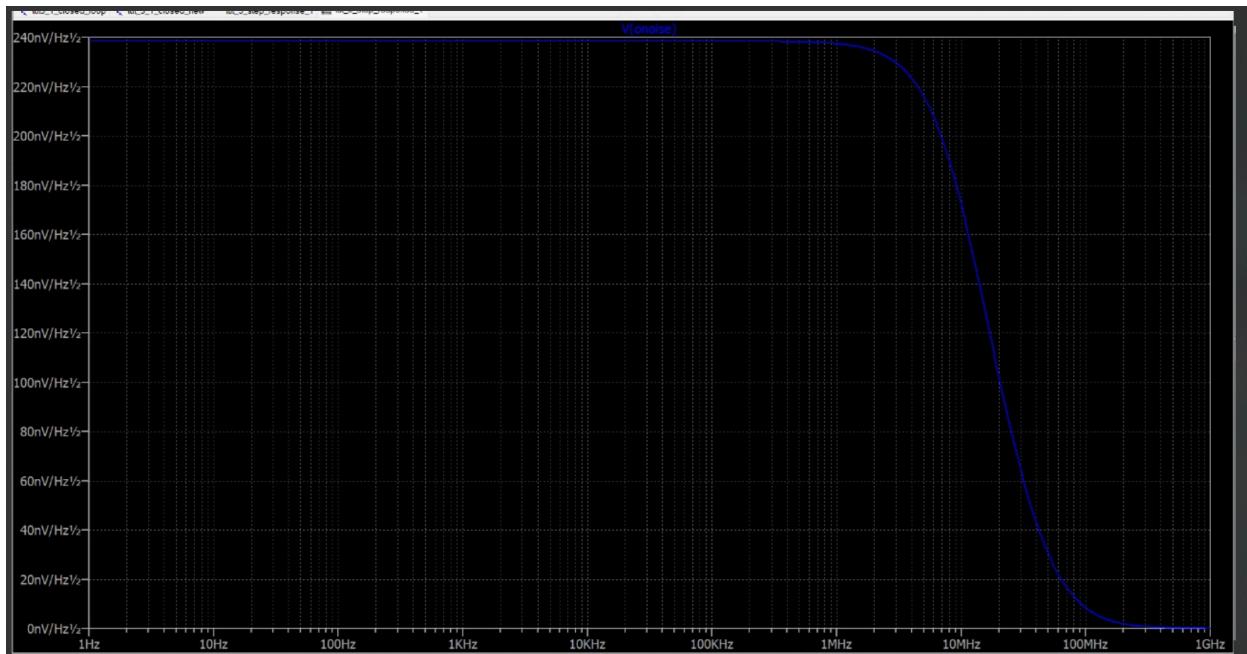


Fig 5: Output Noise PSD (in units)


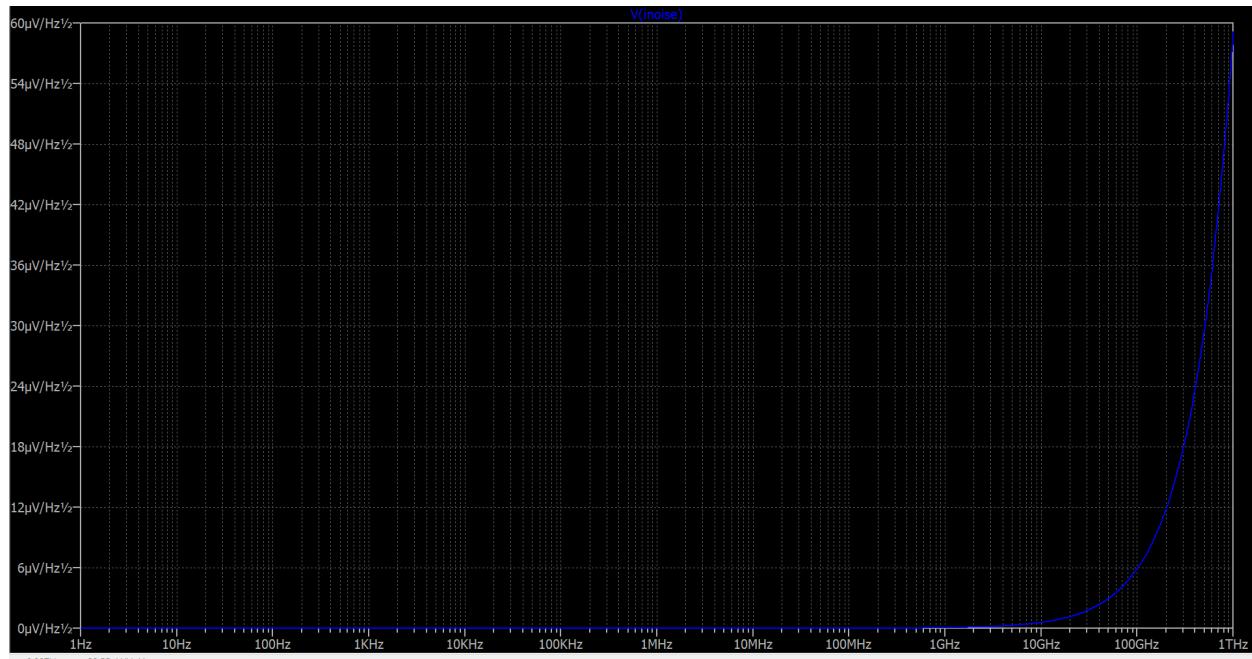


Fig 6: Input Noise PSD

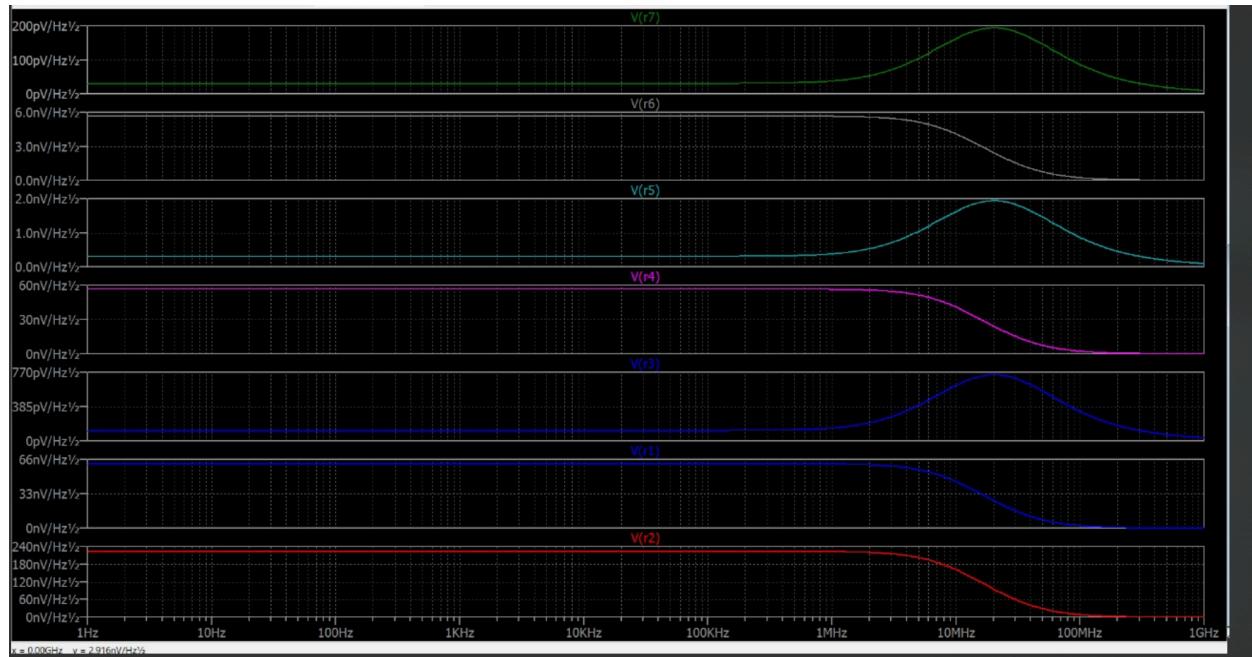


Noise contribution by different resistors

	Obtained Value	Desired Value
--	----------------	---------------


DC Gain	13.29	13
3-dB Bandwidth	10.37 MHz	13MHz
Unity Loop Gain frequency	13.73 MHz	14 MHz
Phase Margin	62.7	
Input Noise PSD at low frequency	0 Hz	
Noise Contribution by R_i (R_2)	223.13685nV/Hz$^{1/2}$	92.9%
Noise Contribution by R_f (R_1)	61.879241nV/Hz$^{1/2}$	25.78%
Noise Contribution by Gm_1 (R_4) R_{N1}	56.581834nV/Hz$^{1/2}$	23.575%
Noise Contribution by Gm_2 (R_5) R_{N2}	309.1015pV/Hz$^{1/2}$	0.128%
Noise Contribution by R_L (R_3)	117.04343pV/Hz$^{1/2}$	0.04875%

Problem 2

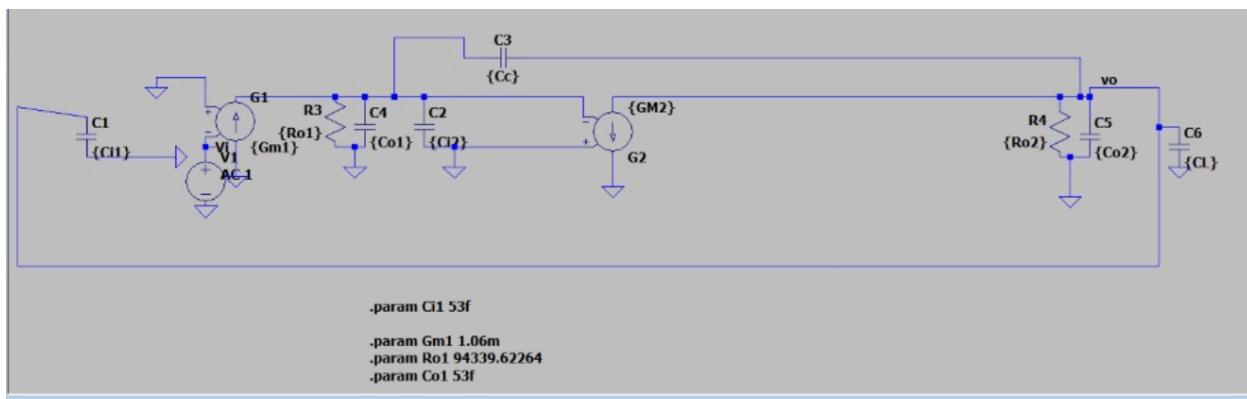


Schematic used for question 2


A) Conventional Miller Opamp

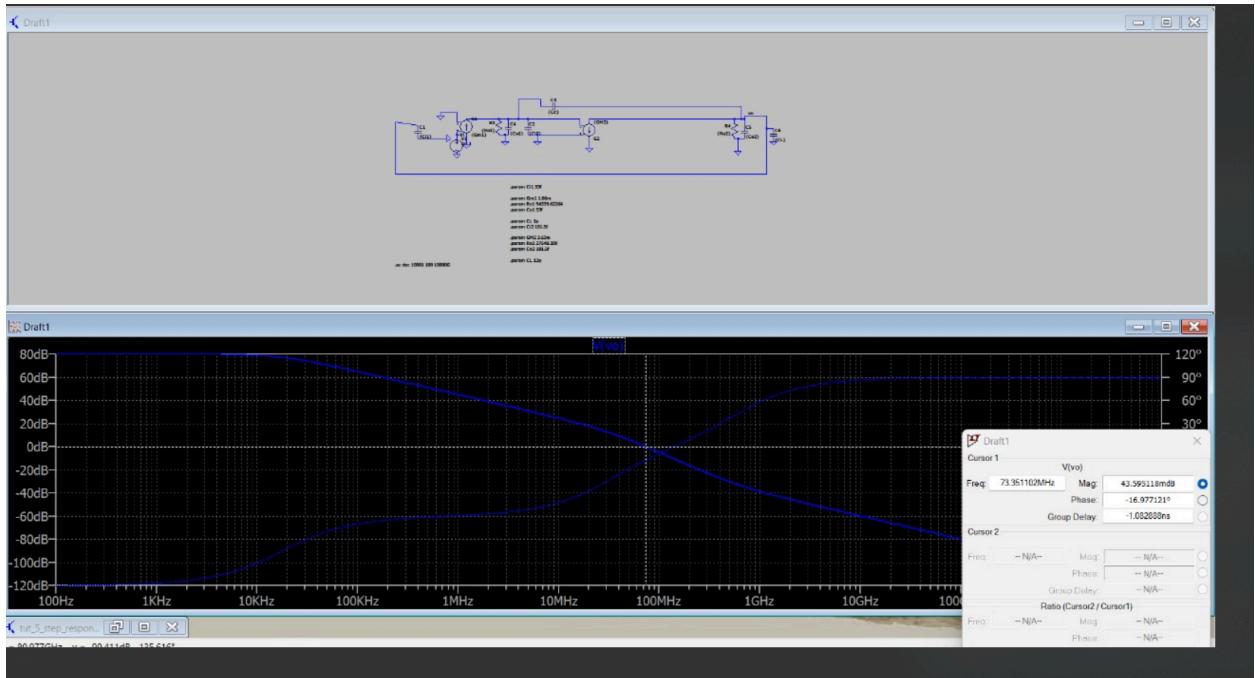

We can see that the voltage gain is close to 0dB, the observed phase margin is equal to 16.97 degrees


B) With R_C in series with C_C

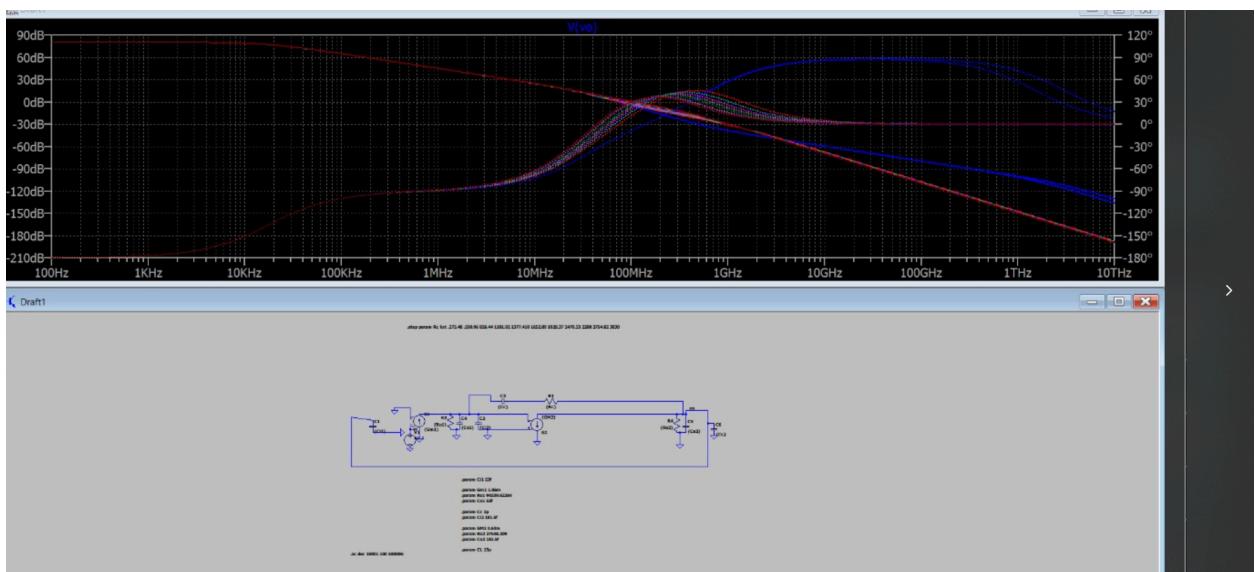

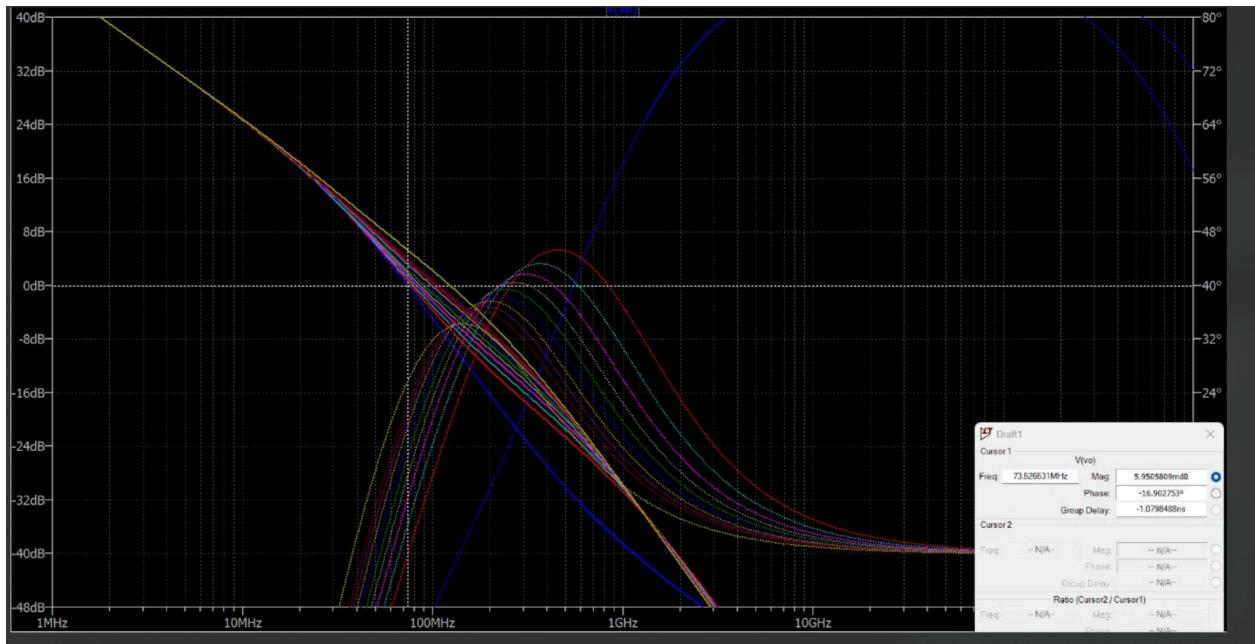


We see that PM increases as R_z increases (pm for different R_z can be seen in left side of the diagram) Hence the optimal value is obtained for $R_z=10/Gm2=2.75$ K ohm for which the phase margin was around 41 degrees.

C) With a unity Gain buffer to drive C_c

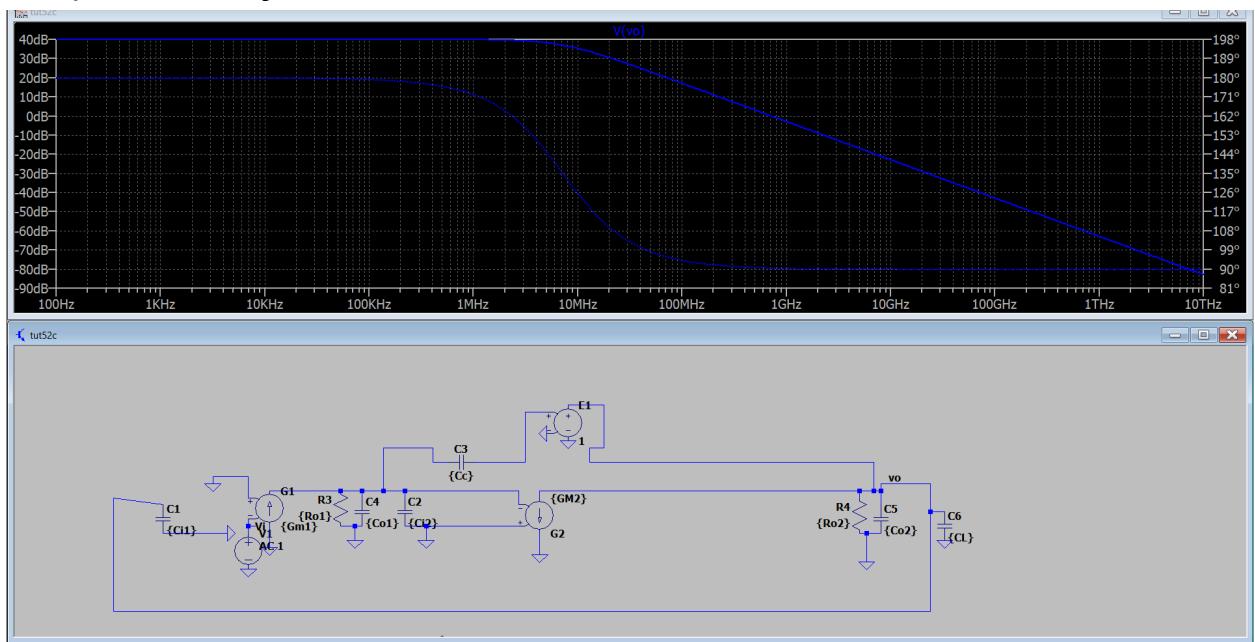

The phase Margin has changed significantly from 5.2 a

D) Use of CCCS

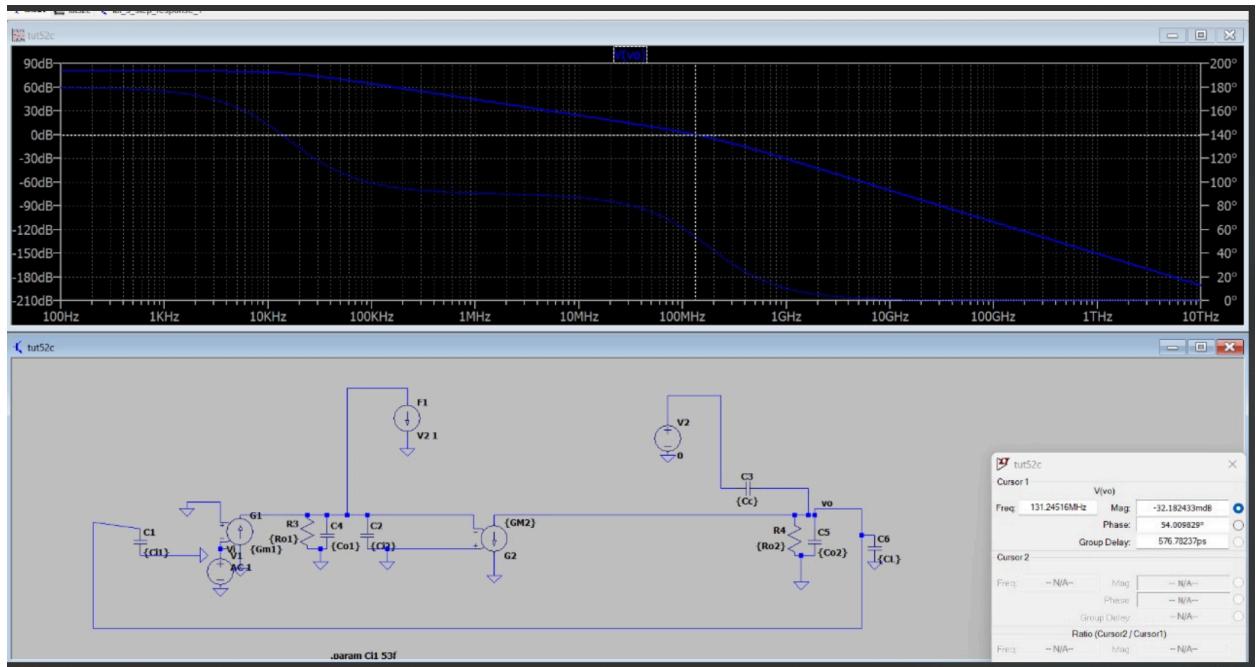


The phase Margin has changed significantly from 5.2 a

Phase margin table:

Circuit	Phase margin in degrees
5.a) Simple miller opamp	16.9
5.b) Miller opamp with R_z	41
5.c) Miller opamp with unity buffer	18
5.d) Miller opamp with cccs	40

Transfer Function

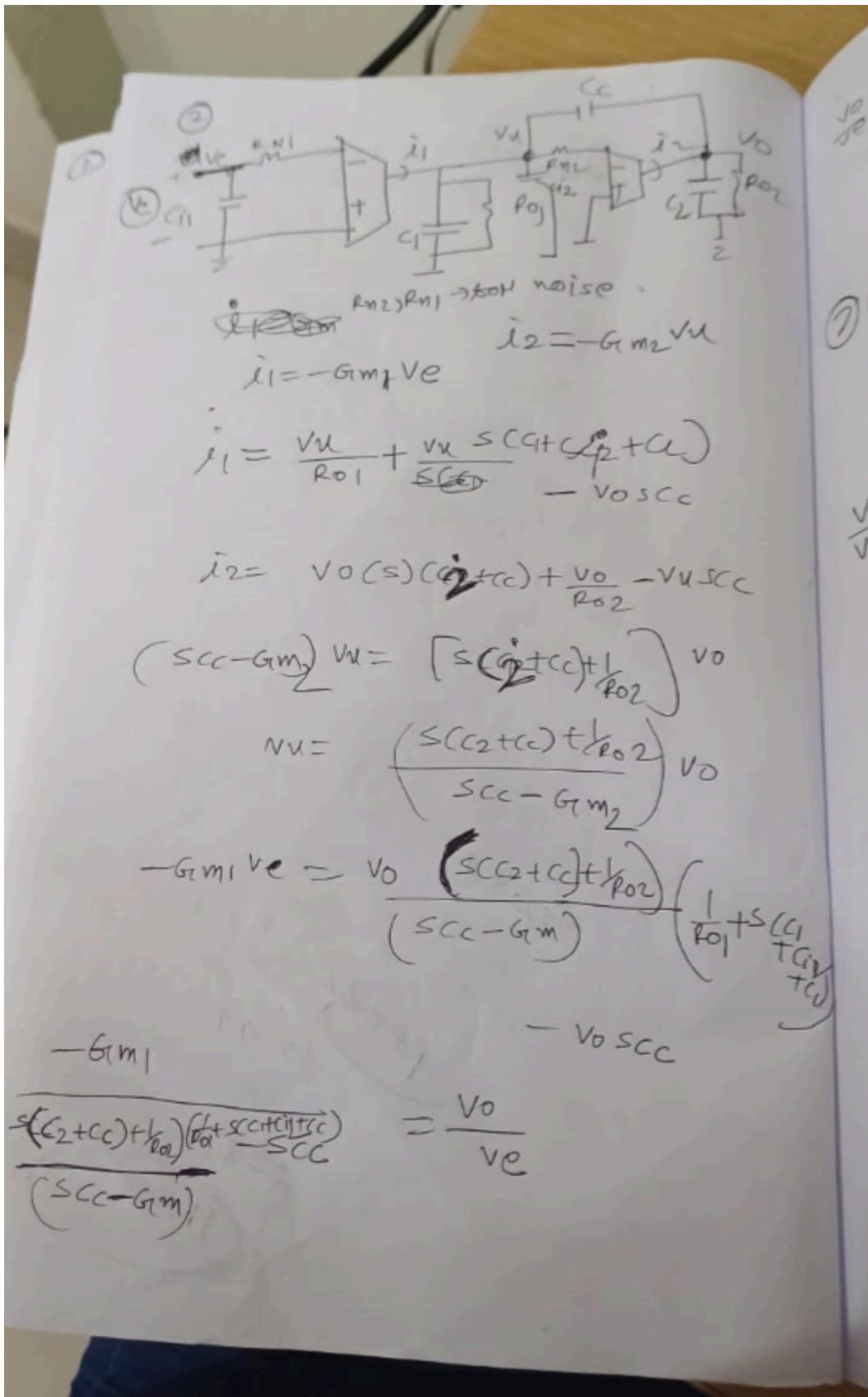

$$\frac{-G_{m1} (S_{CC} - G_m)}{S(C_2 + \frac{C}{1+S_{CC}R_2}) \left(S_{CC}(C + R_1) + \frac{1}{R_{01}} \right) - S_{CC} (S_{CC} - G_m)}$$


⑦(b) by replacing
 $\frac{1}{S_{CC}} \Rightarrow \frac{1}{S_{CC} + R_2}$
 $S_{CC} \Rightarrow \frac{S_{CC}}{1 + S_{CC}R_2}$

$$\frac{V_o}{V_e} = -G_{m1} \times \left(\frac{S_{CC}}{1 + S_{CC}R_2} - G_m \right)$$

$$= \frac{\left[S \left(C_2 + \frac{C}{1 + S_{CC}R_2} \right) \right] \frac{1}{R_{01}}}{\left[S \left(C_1 + \frac{C}{1 + S_{CC}R_2} + (C_2) \right) + \frac{1}{R_{01}} \right] - \frac{S_{CC}}{1 + S_{CC}R_2} \left(\frac{S_{CC}}{1 + S_{CC}R_2} - G_m \right)}$$

$$= \frac{-G_m \left(S (C_{CC} - C_2 R_2 G_m) - G_m^2 \right)}{\left[\left(S (C_1 + C_2 (1 + S_{CC}R_2)) + \frac{1 + S_{CC}R_2}{R_{02}} \right) - S (C_1 + C_2) \frac{S_{CC}R_2 + C}{1 + S_{CC}R_2} \right] \cancel{+ \frac{1}{R_{01}}} }$$
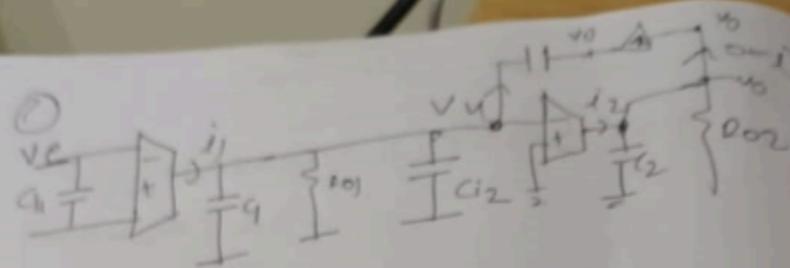
$$\rightarrow S_{CC} \left(\frac{S_{CC}}{1 + S_{CC}R_2} - G_m \right)$$



$$i_1 = -G_{m1} V_e$$

$$i_2 = -G_{m2} V_{out}$$

$$i_1 = V_e (s) (C_1 + C_{i2}) + \frac{V_{out}}{R_{o1}}$$


$$i_2 = V_o s C_2 + \frac{V_o}{R_{o2}}$$

$$-V_e G_{m2} = V_o \left[s C_2 + \frac{1}{R_{o2}} \right]$$

$$V_e = -\frac{V_o \left[s C_2 + \frac{1}{R_{o2}} \right]}{G_{m2}}$$

$$-G_{m1} V_e = -\left(s C_1 + s C_{i2} \right) \frac{1}{R_{o1}} \left(V_o \left[s C_2 + \frac{1}{R_{o2}} \right] \right) \frac{1}{G_{m2}}$$
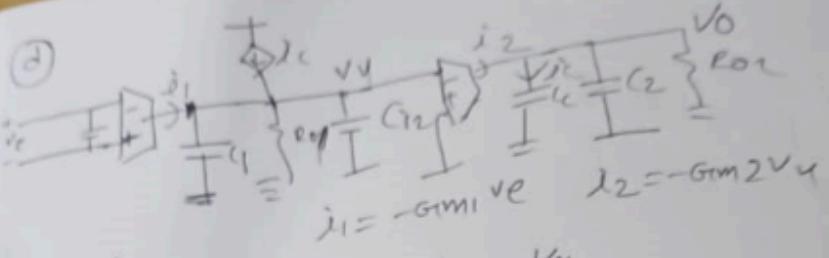
$$\frac{G_{m1} G_{m2}}{\left[s C_1 + s C_{i2} \right] \left[s C_2 + \frac{1}{R_{o2}} \right]} = \frac{V_o}{V_e}$$



$$i_C + i_1 = v_u(s(C_1 + i_2) + \frac{v_u}{R_{02}})$$

$$i_2 = i_C + v_o s C_2 + \frac{v_o}{R_{02}}$$

$$= v_o s C_C$$

$$v_u = -\frac{v_o}{Gm_2} \left[s \gamma (C_2 + C_C) + \frac{1}{R_{02}} \right]$$

$$+ Gm_1 v_e = + \left[s(C_1 + i_2) + \frac{1}{R_{01}} \right] \frac{v_o}{Gm_2} \left(s(C_2 + C_C) + \frac{1}{R_{02}} \right)$$

$\rightarrow v_o s C_C$

$$v_e = v_o$$

$$\frac{v_o}{v_e} = \frac{Gm_1}{s C_C + \frac{1}{Gm_2} \left[s(C_1 + i_2) + \frac{1}{R_{01}} \right] \left[s(C_2 + C_C) + \frac{1}{R_{02}} \right]}$$

$\frac{s^2}{s(R_{02} + 1)}$